

- ① A 3φ, 10kVA, 220V, Y-connected synchronous generator has  $R_a = 0.25\Omega$  per phase and  $X_s = 5.0\Omega$  per phase. Determine the excitation voltage,  $E_f$ , when the generator is delivering full load @ pf of ...

(A)  $\text{pf} = 0.85 \text{ lagging}$


$$S_{\text{rated}} = 10 \text{kVA}$$

$$\text{pf} = 0.85 \text{ lag}$$

$$V_L = 220 \text{V}$$

First, we need the phase voltage at the terminals,  $V_t$ .
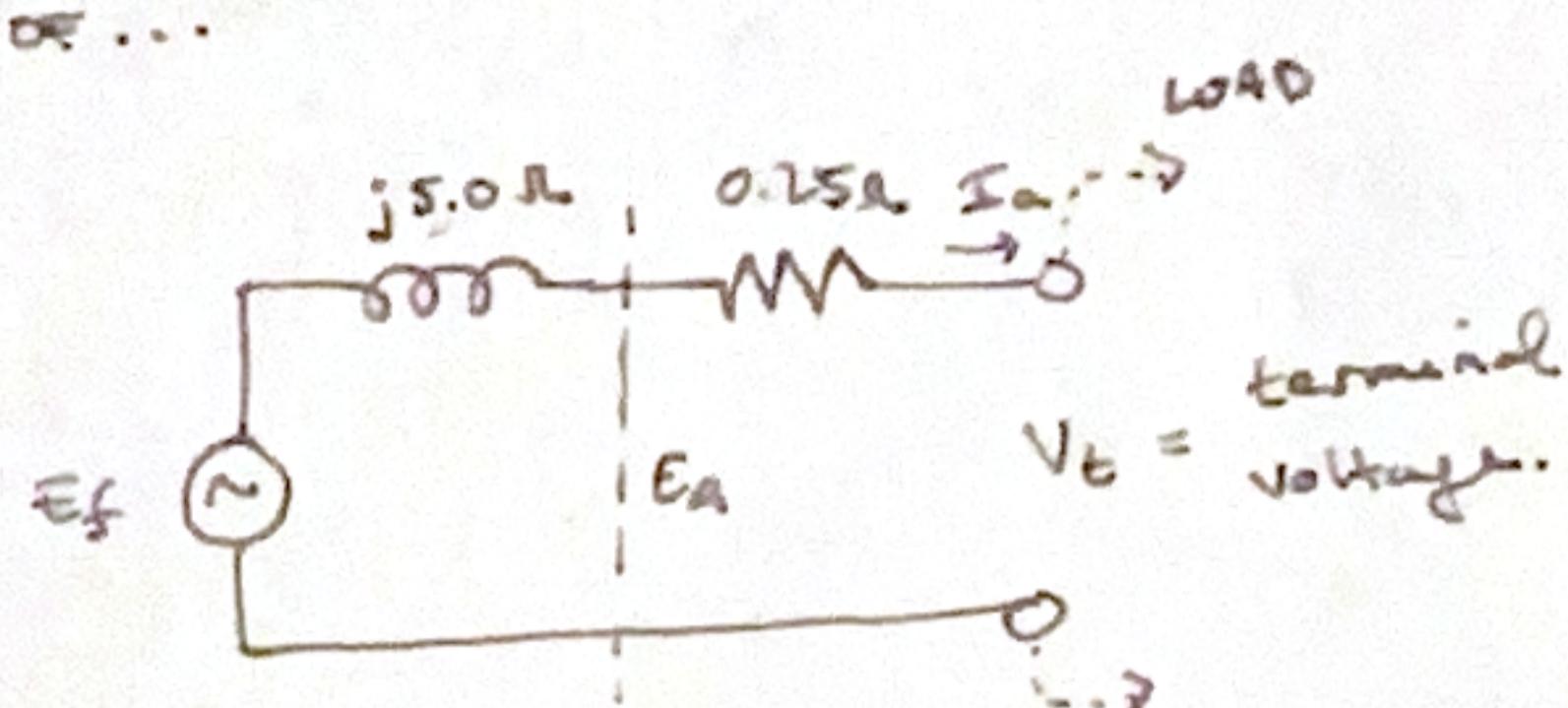
$$V_t = \frac{1}{\sqrt{3}}(220\text{V}) = 127\text{V}$$



From this we can find the current in one phase,  $I_a$ , knowing the rated power 10kVA, and voltage  $V_t = 127\text{V}$ .

$$\Rightarrow |S_{\text{rated}}| = 3N_e I_a \Rightarrow |I_a| = \frac{|S_{\text{rated}}|}{3N_e} = \frac{10 \text{kVA}}{3(127\text{V})} = 26.2 \text{A}$$

$$\text{The phase angle } \theta = \cos^{-1}(0.85) = 31.8^\circ \rightarrow I_a = 26.2 \angle -31.8^\circ \text{ A}$$

$\downarrow$   
negative since current lags in lagging load.

KVL

$$-E_f + I_a(0.25 + j5.0) + V_t = 0$$

$$\Rightarrow E_f = (26.2 \angle -31.8^\circ)(0.25 + j5.0) + 127 \\ = 228.65 \angle 28.2^\circ \text{ V}$$

(B)  $\text{pf} = 1.0$

$$\theta = \cos^{-1}(1.0) = 0^\circ \therefore I_a = 26.2 \angle 0^\circ \text{ A}$$

$$\Rightarrow E_f = (26.2 \angle 0^\circ)(0.25 + j5.0) + 127 \\ = 187.1 \angle 44.4^\circ \text{ V}$$

(C)  $\text{pf} = 0.2 \text{ leading}$

$$\theta = \cos^{-1}(0.2) = 76.9^\circ, \text{ leading so current leads} \therefore \theta_i = 36.9^\circ \text{ as well} \therefore I_a = 26.2 \angle 36.9^\circ \text{ A}$$

$$\Rightarrow E_f = (26.2 \angle 36.9^\circ)(0.25 + j5.0) + 127 \\ = 121.2 \angle 43.3^\circ \text{ A}$$

② A 3 $\phi$ , 14 kV, 10 MVA, 60 Hz, 2 pole, 0.85 pf lagging, Y-connected synchronous generator has  $X_s = 20\Omega$  per phase and  $R_s = 2\Omega$  per phase.

The generator is connected to an infinite bus.

- (a) DETERMINE THE EXCITATION VOLTAGE AT THE RATED CONDITION.  
DRAW THE PHASOR DIAGRAM.

$$P=2$$

$$\text{pf} = 0.85 \text{ lag}$$

$$S_{\text{rated}} = 10 \text{ MVA}$$

$$V_L = 14 \text{ kV}$$

$$V_t = \frac{1}{\sqrt{3}} (14 \text{ kV}) = 8.083 \text{ kV}$$

$$|I_{\text{ad}}| = \frac{|S_{\text{rated}}|}{3|V_t|} = \frac{10 \text{ MVA}}{3(8.083 \text{ kV})} = 412.4 \text{ A}$$

$$\theta_I = -\theta = -\cos^{-1}(0.85) = -31.3^\circ$$

$\rightarrow$

b1 = lagging


$$I_a = 412.4 L -31.3^\circ \text{ A}$$

[EFL]

$$E_f = (412.4 L -31.3^\circ)(2 + j20) + 8.083 \text{ kV}$$

$$= 14.68 L 26.6^\circ \text{ kV}$$

From the above  $|E_f| L \delta \Rightarrow |E_f| = 14.68 \text{ kV}, \delta = 26.6^\circ$

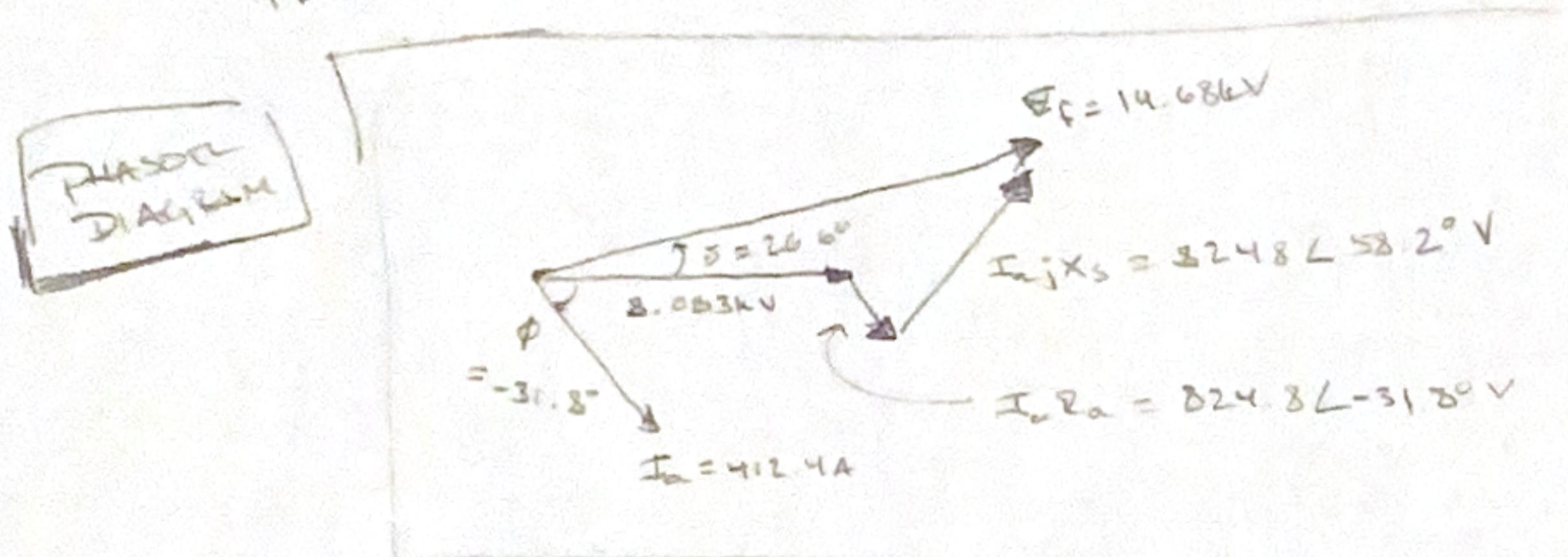


- (b) DETERMINE POWER (TORSION) ANGLE AT RATED CONDITION.

$\delta$  is the power torsion angle, which above

$$\delta = 26.6^\circ$$

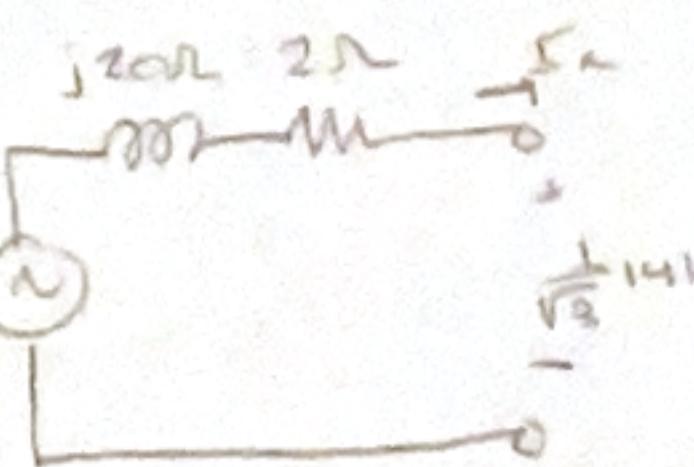- (c) IF FIELD CURRENT IS CONSTANT, DETERMINE THE MAX POWER THE GENERATOR CAN SUPPLY.

$$P_{\text{max}} = \frac{3E_f V_t}{X_s} = \frac{3(14.68 \text{ kV})(8.083 \text{ kV})}{20\Omega} = 17.8 \text{ MW}$$



has no  
phase angle  
so nearly  
 $V_t = 8.083 L 0^\circ$   
kV