

ECE 385 – Fall 2024

Instructor: Michael Abba

TA: Bishal Lamichhane

HW #2

Due Date: Uploaded to D2L by 10 PM Friday September 20, 2024

Problem 1

A single-phase transformer has 500 turns in the primary winding. When it is connected to a single-phase, 120 [V], 60 [Hz] power supply, the no-load current is 1.6 [A] and the no-load power is 80 [W]. Neglect the winding resistance and leakage reactance.

Calculate:

- the core loss current, I_c ,
- the magnetizing current, I_m ,
- the peak value of the core flux, ϕ_{max} ,
- the magnetizing reactance, X_m , and core loss resistance, R_c .

Problem 2

A single-phase, 10 [kVA], 2400/120 [V], 60 [Hz] transformer has the following equivalent circuit parameters:

- $Z_{eq,H} = 5 + j25 [\Omega]$
- $R_{c,H} = 64 [k\Omega]$
- $X_{m,H} = 64 [k\Omega]$

where subscript H represents the values referred to high-voltage side. Standard no-load and short-circuit tests are performed on this transformer. Determine the following:

- No-load test results : V_{oc} , I_{oc} , and P_{oc}
- Short-circuit test results : V_{sc} , I_{sc} , and P_{sc}


Problem 3

A single-phase, 1200 [kVA], 240/120V, 60 [Hz] transformer has a no load loss of 3.2 [kW] at rated voltage and a copper loss of 9.5 [kW] at rated current. Determine the efficiency for the following load conditions:

- 1200 [kVA] at unity power factor.
- 1200 [kVA] at 0.9 power factor.
- 1200 [kVA] at 0 power factor (i.e., pure L or C load).

Problem 4

A 120-V AC supply delivers power to a load modeled as a $5\text{-}\Omega$ resistance in series with a $3\text{-}\Omega$ inductive reactance. Find the active, reactive, and apparent power consumption of the load along with its power factor. Draw its power triangle.

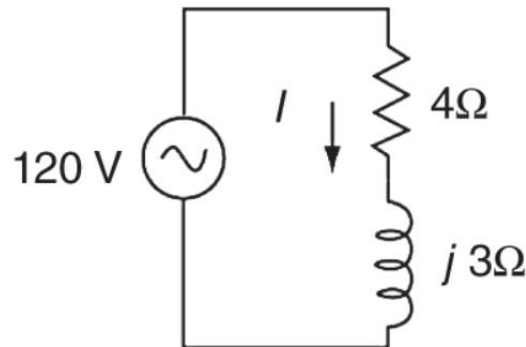

Problem 5

Three 1ϕ , 10 kVA, 460/120 V, 60 Hz transformers are connected to form a 3ϕ , 460/208 V transformer bank. The equivalent impedance of each transformer referred to the high-voltage side is $1.0 + j2.0\,\Omega$. The transformer delivers 20 kW at 0.8 power factor (leading).

- (a) Draw a schematic diagram showing the transformer connection.
- (b) Determine the transformer winding current.
- (c) Determine the primary voltage.
- (d) Determine the voltage regulation.

Problem 6

Two identical 250 kVA, 230/460 V transformers are connected in open delta to supply a balanced 3ϕ load at 460 V and a power factor of 0.8 lagging. Determine

- (a) The maximum secondary line current without overloading the transformers.
- (b) The real power delivered by each transformer.
- (c) The primary line currents.
- (d) If a similar transformer is now added to complete the Δ , find the percentage increase in real power that can be supplied. Assume that the load voltage and power factor remain unchanged at 460 V and 0.8 lagging, respectively.