

## ECE 385 – Fall 2024

Instructor: Michael Abba

TA: Bishal Lamichhane

### HW #7

*Due Date: Uploaded to D2L by 10 PM Friday December 6, 2024*

---

#### Problem 1 (10 points)

A 3  $\phi$ , 10 kVA, 220 V, Y-connected synchronous generator has  $R_a = 0.25 \Omega$  per phase and  $X_s = 5.0 \Omega$  per phase. Determine the excitation voltage,  $E_f$ , when the generator is delivering full load at power factor of

- a) 0.85 lagging.
- b) unity.
- c) 0.8 leading.

#### Problem 2 (10 Points)

A 3 $\phi$ , 14 kV, 10 MVA, 60 Hz, two-pole, 0.85 PF lagging, Y-connected, synchronous generator has  $X_s = 20 \Omega$  per phase and  $R_s = 2 \Omega$  per phase. The generator is connected to an infinite bus.

- a) Determine the excitation voltage at the rated condition. Draw the phasor diagram for this condition.
- b) Determine the power (torque) angle at the rated condition.
- c) If the field current is kept constant, determine the maximum power the generator can supply.

#### Problem 3 (30 points)

Research the Northeast blackout of 2003 discussed in class. Briefly explain the following:

- a) What caused the outage?
- b) What factors contributed to the duration and size of the outage?
- c) How did the use of the Infinite Bus (or grid) system studied in class contribute to the outage and/or limit the outage?
- d) What learnings came from the outage related to technical, operational, and ethical considerations for engineers?