

INTRODUCTORY LTSPICE SIMULATIONS


ENERGY HARVESTING

EH-202420


GRACE DODD, AARON FAIVRE, CHASE LOTITO

Circuit I - Schematic

- Switching element on bottom of primary coil, 50% duty cycle.
- After 100ms, $V_L=46.65\text{V}$, $I_L=466.5\mu\text{A} \rightarrow P_L=21.7\text{mW}$ (Spot on with 2nd paper.)

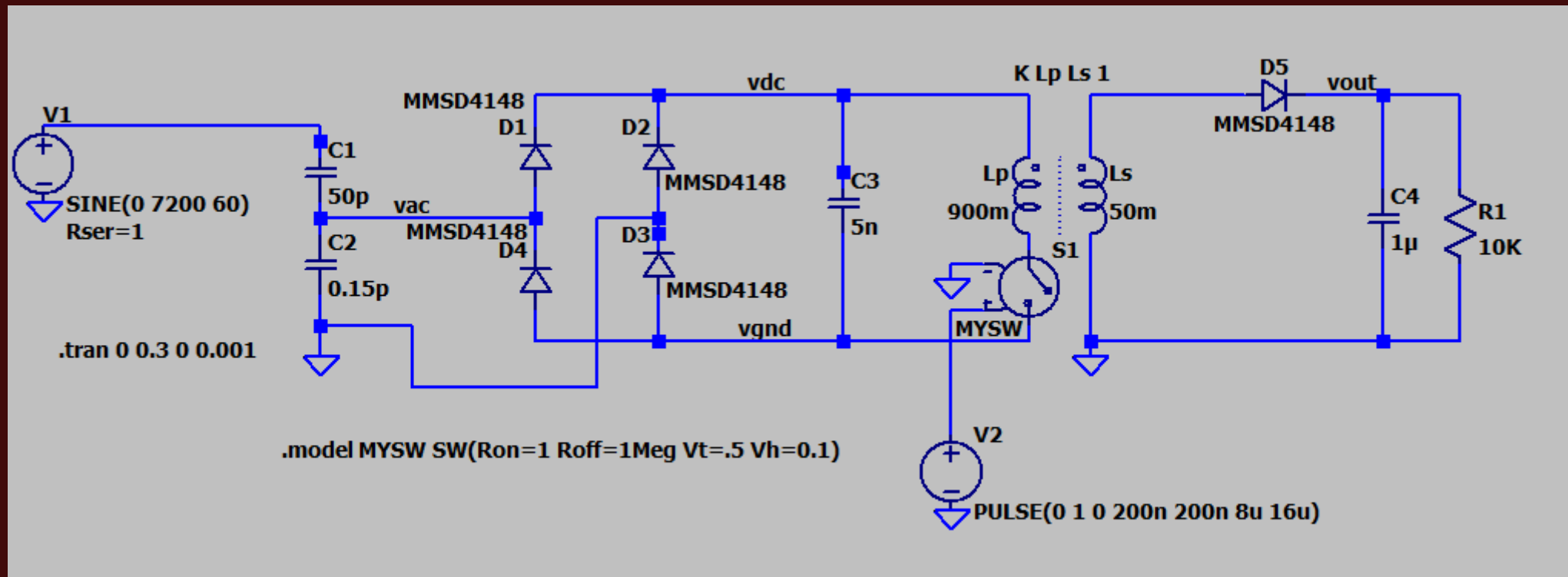


Circuit I - Waveforms

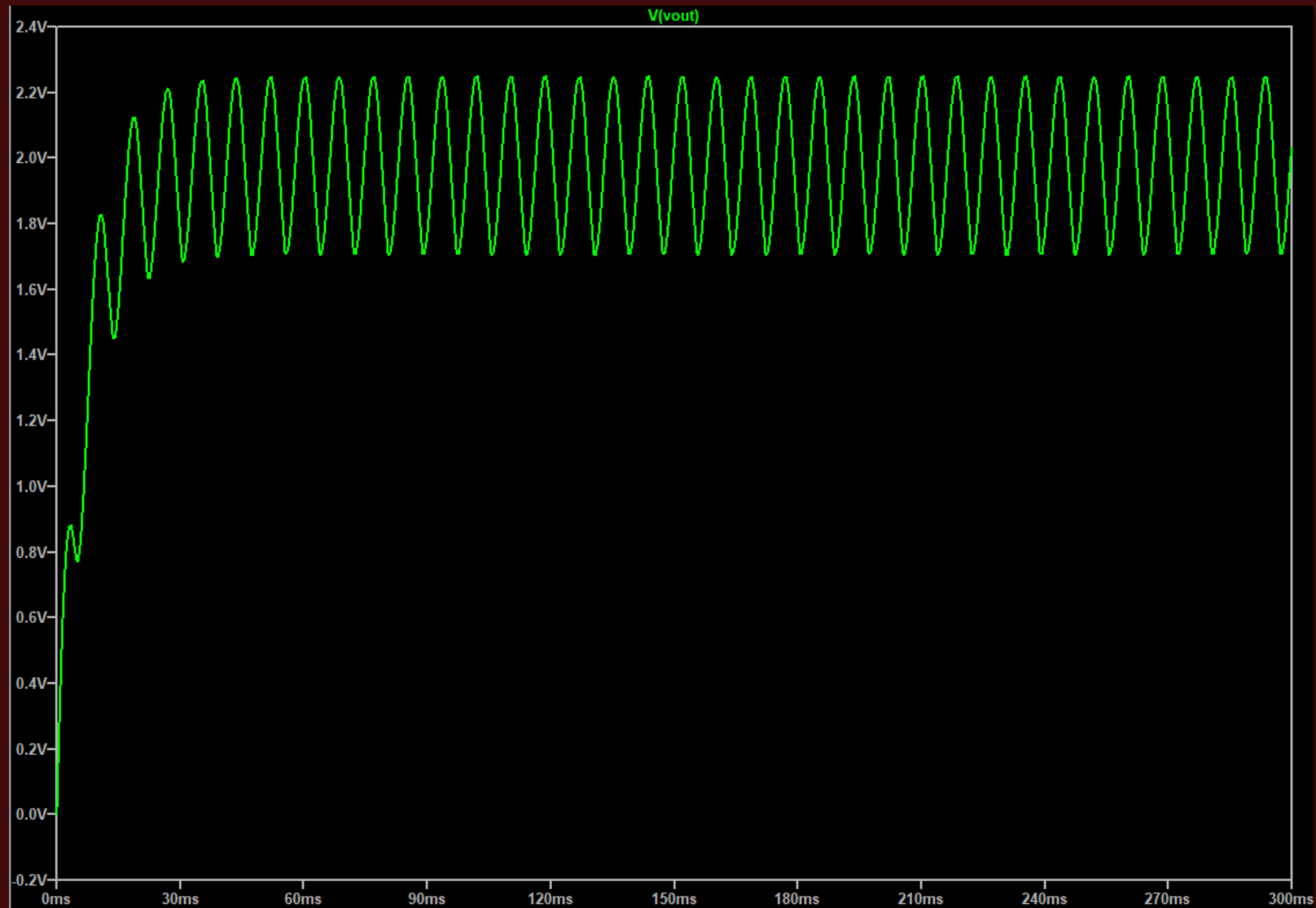

Circuit I – Waveforms (cont.)

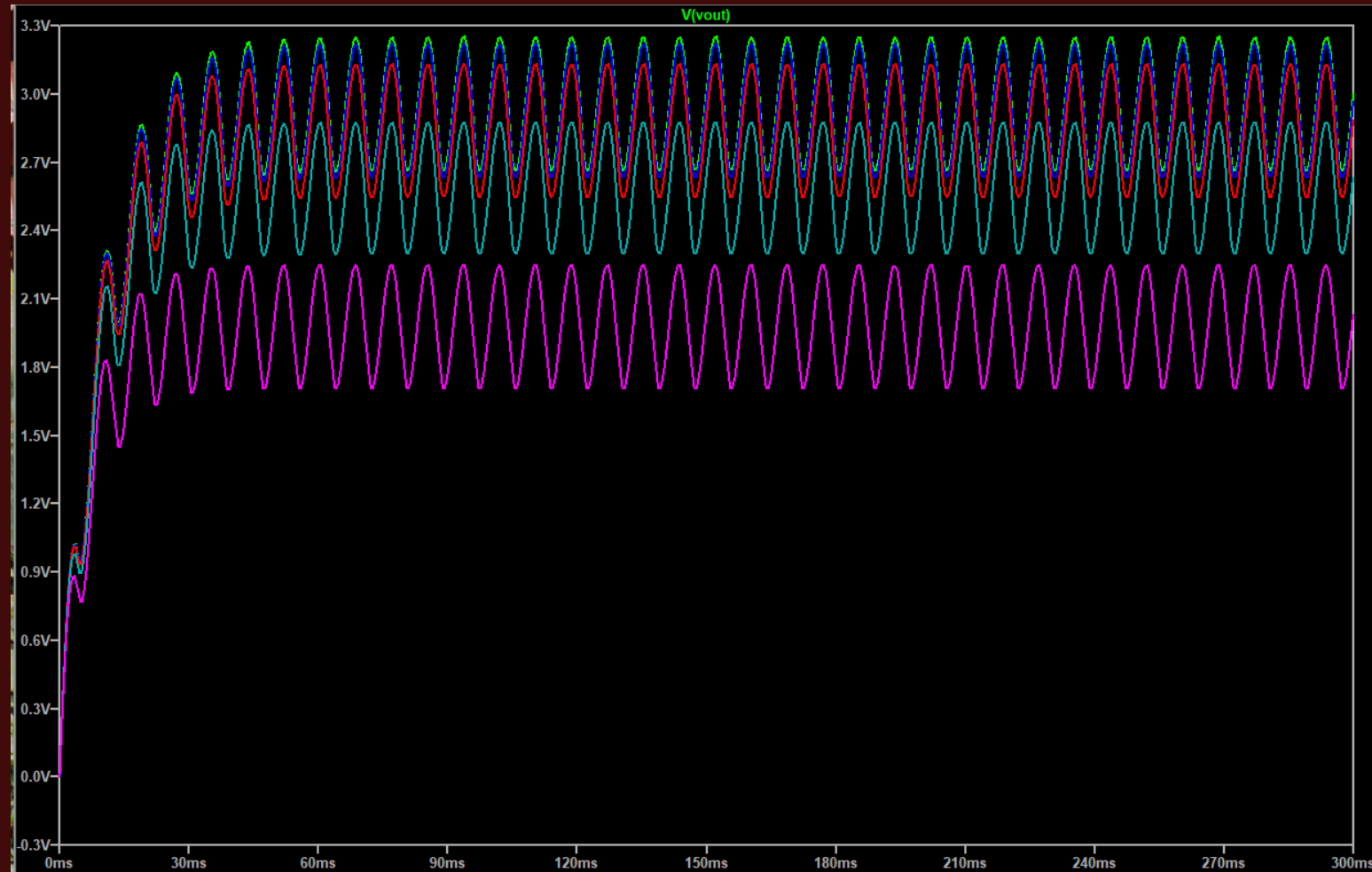
Doing a parametric sweep of the switching element's on-time, i.e. a sweep of duty cycle.



Increasing
Duty
Cycle


Circuit II - Schematic

- Switching element on top of primary coil, 3.125% duty cycle.
- Second rectifier on secondary side.
- After 100ms, $V_L=46.65\text{V}$, $I_L=466.5\mu\text{A} \rightarrow P_L=21.7\text{mW}$ (Spot on with 2nd paper.)

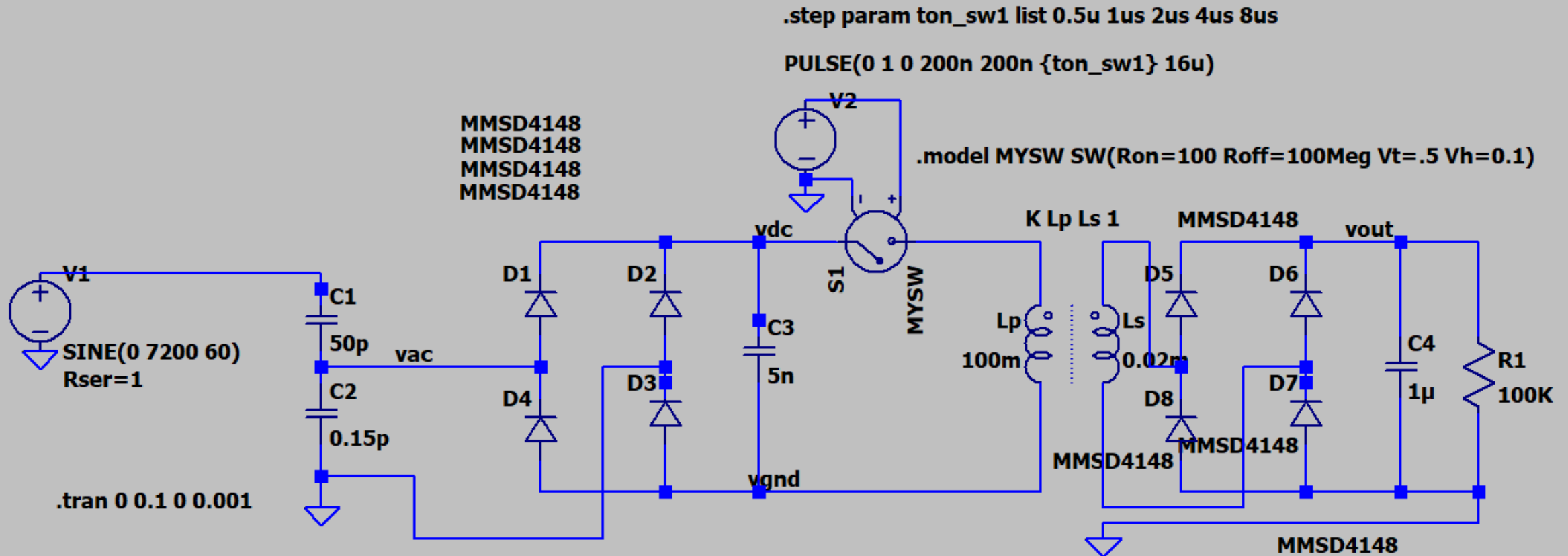

Circuit II - Waveforms

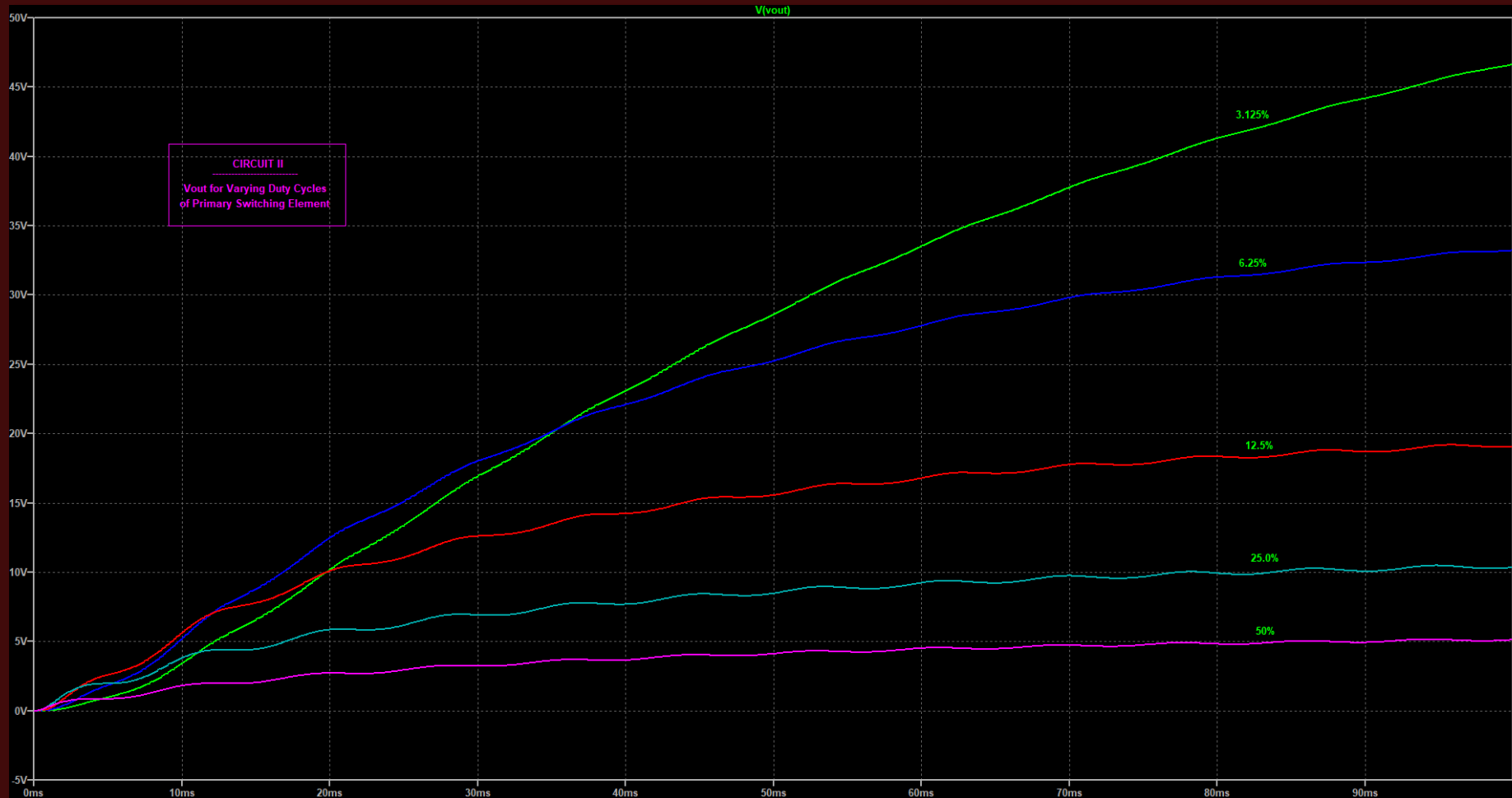
A more effective parametric sweep of switching duty cycle.




Smaller duty cycles increase power extraction.

Circuit III - Schematic

- Zangl Topology: Taking PWS input off C1 (Harvester Capacitance)
- Much harder to get clean simulations.

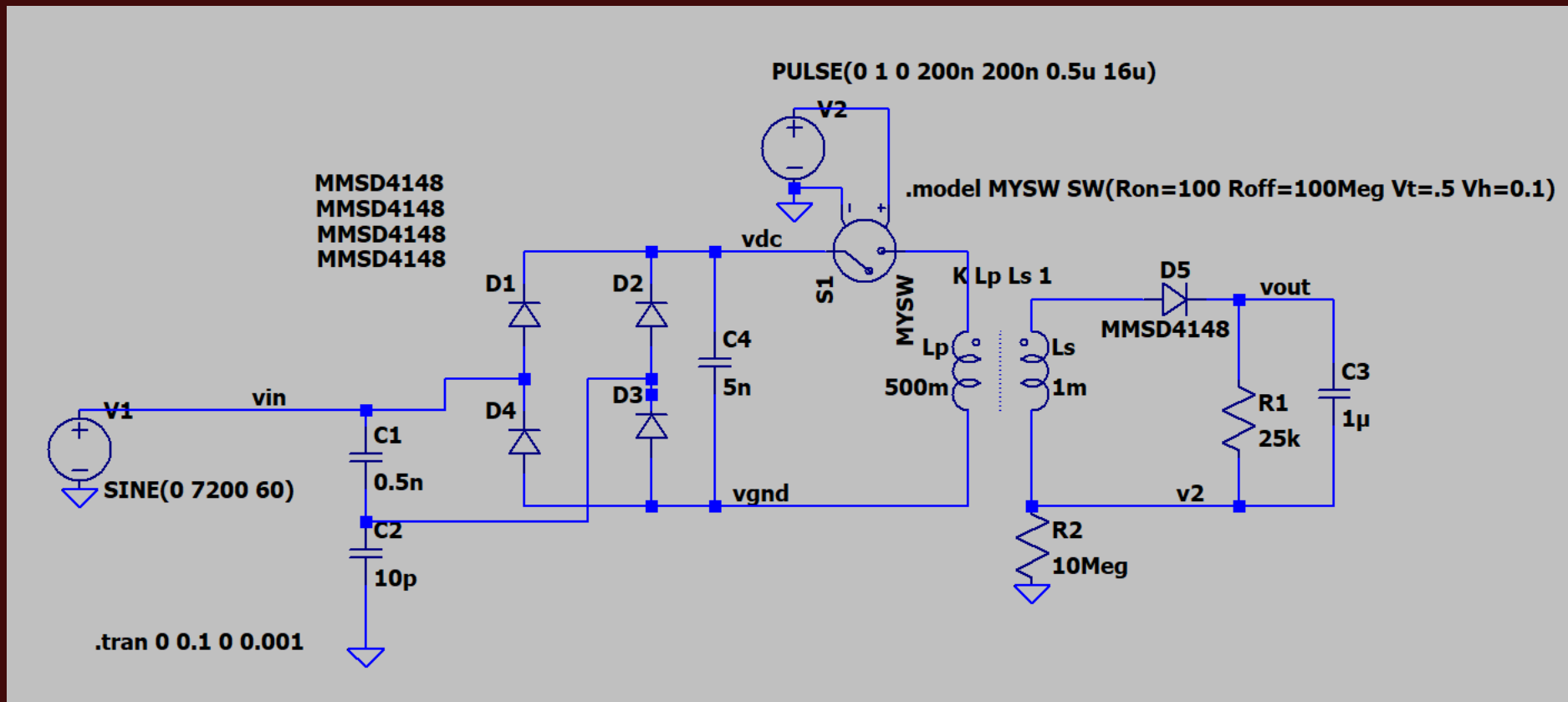

Circuit III - Waveforms

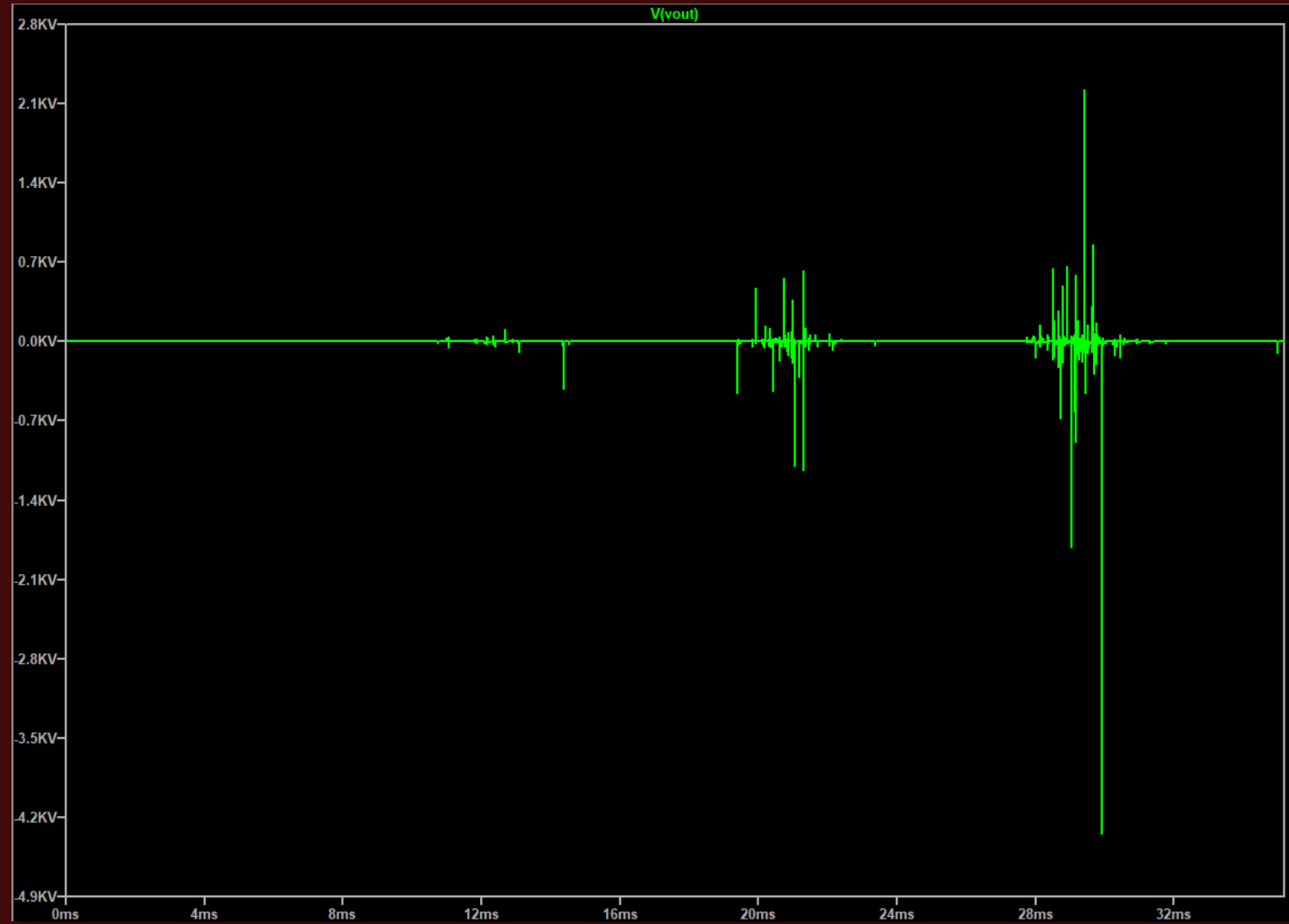

Circuit III - Waveforms

- Increasing $C_1=35\text{nF}$,
we can get
 $V_{\text{out}}=1.91\text{mV}$,
 $I_L=75.95\text{nA}$,
 $P_{\text{out}}=145\text{pW}$

