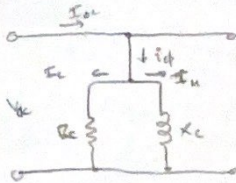


- 1) $1\text{-}\phi$ XF HAS 500 TURNS IN PRIMARY WINDING. WHEN CONNECTED TO 1ϕ , 120V, 60Hz PWS, THE NO-LOAD CURRENT IS 1.6A AND THE NO-LOAD POWER IS 30W. NEGLECT WINDING RESISTANCE + LEAKAGE RESISTANCE.

CALCULATE:

- CORE LOSS COEFFICIENT, I_c
- MAGNETIZING CURRENT, I_m
- PEAK VALUE OF CORE FLUX, ϕ_{max}
- R_c, X_m .

* remember these are magnitudes of phasors.



$$V_c = 120V$$

$$I_0 = 1.6A$$

$$P_c = 30W$$

$$P_c = \frac{V_c^2}{R_c} = 180\Omega$$

$$\Rightarrow I_c = \frac{V_c}{R_c} = \frac{120}{180} = 0.667A$$

$$\Rightarrow I_m = \sqrt{(1.6)^2 - (0.667)^2} = 1.45A$$

$$\Rightarrow X_m = \frac{V_c}{I_m} = \frac{120}{1.45} = 82.8\Omega$$

$$Z_c = \frac{j\omega L}{2\pi f}$$

$$\Rightarrow X_m = 2\pi f L_m = 2\pi f \frac{N\phi_{max}}{I_m} \Rightarrow \phi_{max} = \frac{X_m I_m}{2\pi f N} = \frac{(82.8)(1.45)}{2\pi(60)(500)} = 1.94\mu Wb$$

$$\therefore \begin{cases} I_c = 0.667A \\ I_m = 1.45A \\ \phi_{max} = 703\mu Wb \\ R_c = 180\Omega \\ X_m = 82.8\Omega \end{cases}$$


$$\phi_{max} = \frac{E_{rms}}{4.44Nf}$$

- 2) 1ϕ , 10kVA, 2400/120V, 60Hz, TRANSFORMER HAS THE FOLLOWING NO-LOAD PARAMETERS:

$$\begin{aligned} Z_{0,H} &= 5 + j25\Omega & \text{turns ratio } a &= \frac{2400}{120} = 20 \\ R_{0,H} &= 64k\Omega \\ X_{0,H} &= 64k\Omega \end{aligned}$$

DETERMINE: NO-LOAD TEST RESULTS (V_{0L}, I_{0L}, P_{0L}) + SHORT-CIRCUIT TEST RESULTS (V_{sc}, I_{sc}, P_{sc}).

NOLOAD \rightarrow Low-Side

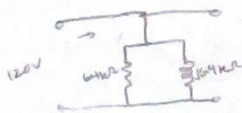

$$V_{0L} = 120V \text{ (rated)}$$

$$P_{0L} = \frac{120^2}{160} = 90W$$


$$R_{0L} = \frac{1}{a^2} R_{0,H} = \frac{1}{20^2} (64k) = 160\Omega$$

$$X_{0L} = \frac{1}{a^2} X_{0,H} = 160\Omega$$

$$Q_{0L} = \frac{P_{0L}}{I_{0L}} = 90VAR \Rightarrow I_{0L} = \sqrt{\frac{P_{0L}}{Q_{0L}}} = 0.75A, \quad I_{0L} = \sqrt{(0.75)^2 + (1.06)^2} = 1.06A$$

$$\begin{cases} V_{0L} = 120V \\ I_{0L} = 1.06A \\ P_{0L} = 90W \end{cases}$$

SHORT-CIRCUIT

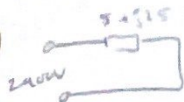

$$\Rightarrow I_{sc} = \frac{S_{rated}}{V_{sc}} = \frac{10k}{2400} = 4.17A$$

$$P_{sc} = 5\Omega = R_{0L} \{Z_{0L}\} \Rightarrow P_{sc} = I^2 R = (4.17)^2 (5) = 86.9W$$

$$|Z_{0L}| = \sqrt{5^2 + 25^2} = 25.5\Omega$$

$$\Rightarrow V_{sc} = I_{sc} |Z_{0L}| = (4.17)(25.5) = 106.3V$$

$$\begin{cases} V_{sc} = 106.3V \\ I_{sc} = 4.17A \\ P_{sc} = 86.9W \end{cases}$$

Voltage needs full impedance

③ 1 ϕ , 1200kVA, 240/120V, 60Hz ~~Power~~ Transformer has a no-load loss of

3.2kW @ V_{rated} and a copper loss of 7.5kW @ I_{rated} . Determine efficiency

for the following load conditions.

- 1200kVA @ $pf=1.0$
- 1200kVA @ $pf=0.9$
- 1200kVA @ $pf=0.0$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{cu} + P_{core}}$$

$$P_{cu} = I_1^2 R_{eq1} + I_2^2 R_{eq2}$$

$$= I_1^2 R_{eq1}$$

$$= I_2^2 R_{eq2}$$

$$P_{out} = V_2 I_2 \cos \theta_2$$

$$\eta = \frac{V_2 I_2 \cos \theta_2}{V_2 I_2 \cos \theta_2 + P_c + I_2^2 R_{eq2}}$$

PRELIMINARY INFO

$$S_{rated} = 1200 \text{ kVA}$$

$$V_{rated,H} = 240 \text{ V}$$

$$V_{rated,L} = 120 \text{ V}$$

$$I_{rated,H} = 5 \text{ kA}$$

$$I_{rated,L} = 10 \text{ kA}$$

$$P_{core} = 3.2 \text{ kW} \text{ by definition}$$

$$P_{cu} = 7.5 \text{ kW} \text{ by definition}$$

When $pf=1$, then $P_c = P_w \therefore P_c = P_{cu} = 3.2 \text{ kW}$

$$\Rightarrow P_{out} = V_2 I_2 \cos \theta_2 = |S_{rated}| (1) = 1200 \text{ kW}$$

$$\Rightarrow \eta_{pf=1} = \frac{1200 \text{ kW}}{1200 \text{ kW} + 3.2 \text{ kW} + 7.5 \text{ kW}} = 0.9895 \therefore \boxed{\eta_{pf=1} = 98.95\%}$$

When $pf=0.9$

$$\Rightarrow P_{out} = |S_{rated}| \cos \theta_2 = (1200 \text{ kVA})(0.9) = 1080 \text{ kW}$$

$$\Rightarrow \eta_{pf=0.9} = \frac{1080 \text{ kW}}{1080 \text{ kW} + 3.2 \text{ kW} + 7.5 \text{ kW}} = 0.9884 \therefore \boxed{\eta_{pf=0.9} = 98.84\%}$$


When $pf=0.0$

$$\Rightarrow P_{out} = |S_{rated}| \cos \theta_2 = (1200 \text{ kVA})(0) = 0$$

$$\Rightarrow \eta_{pf=0} = \frac{0}{0 + 3.2 \text{ kW} + 7.5 \text{ kW}} = 0.0 \therefore \boxed{\eta_{pf=0} = 0.0\%}$$

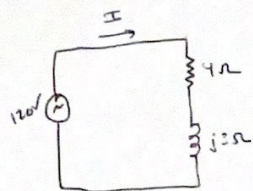PROBLEM 4

FIND ACTIVE, REACTIVE, & APPARENT POWER CONSUMPTION OF THE LOAD (& pf). Draw its power triangle.



CURRENT

$$I = \frac{V}{Z} = \frac{120}{4 + j3} = 24 \angle -36.9^\circ \text{ A} \quad \therefore |I| = 24 \text{ A}$$

ACTIVE

$$P = |I|^2 R = (24)^2 (4) = 2304 \text{ W}$$

REACTIVE


$$Q = |I|^2 X = (24)^2 (3) = 1728 \text{ VAR}$$

APPARENT

$$|S| = \sqrt{P^2 + Q^2} = \sqrt{2304^2 + 1728^2} = 2880 \text{ VA}$$

$$\Rightarrow pf = \frac{P}{S} = \frac{2304}{2880} = 0.8$$

$$\Rightarrow pf = 0.8 \text{ lag}$$

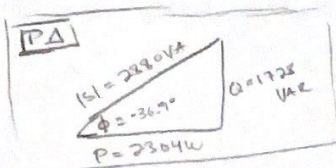


PROBLEM 5

THREE 1φ, 10kVA, 460/120V XFMS FORM A 3φ 460/208V XF. ZED FOR EACH XF ON THE HIGH SIDE IS $1.0 + j2.0 \Omega$. THE 3φ XF SERVES A 20kW LOAD @ 0.8 pf leading.

SCHEMATIC

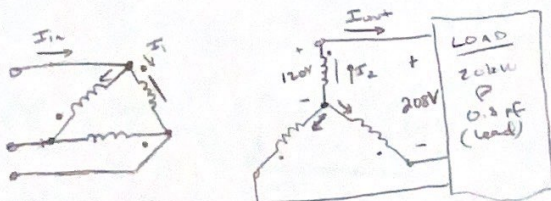SINCE PRIMARY VOLTAGE FROM 1φ → 3φ IS THE SAME AND THE SECONDARY VOLTAGE FROM 1φ → 3φ INCREASED, IT IS A Δ-Y CONFIG.



WINDING CURRENT

$$S_{\text{WIND}} = \frac{P_{\text{LOAD}}}{pf} = \frac{20 \text{ kW}}{0.8} = \frac{20 \text{ kW}}{4/5} = 25 \text{ kVA}$$

THE SECONDARY COIL WINDING SERVES THE LOAD $\therefore I_2 = I_{\text{out}}$.

$$\text{FOR 3φ SYSTEMS } \tilde{S} = \sqrt{3} \tilde{V} \tilde{I}. \quad \therefore |I| = \frac{|\tilde{S}|}{\sqrt{3} \tilde{V}} = \frac{25 \text{ k}}{\sqrt{3} 208} = 69.4 \text{ A} \quad \therefore I_2 = 69.4 \text{ A}$$

FOR THE PRIMARY COIL,


$$I_1 = \frac{1}{a} I_2 = \left(\frac{460}{120} \right) (69.4) = 18.1 \text{ A} \quad \rightarrow I_1 = 18.1 \text{ A}$$

CONTINUED



PRIMARY VOLTAGE

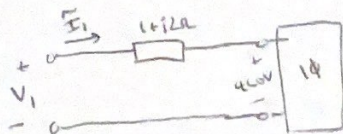TO FIND THE PRIMARY VOLTAGE, WE HAVE TO ANALYZE
A SINGLE ϕ ON THE HIGH SIDE, WHERE $Z_{eq,H} = 1 + j2\Omega$.



FIRST, WE USED THE PHASE ON THE CURRENT

$$\rightarrow \phi = \cos^{-1}(0.8) = 36.9^\circ, \text{ but } \phi < 0 \text{ b/c LEADING.}$$

$$\phi = \phi_V - \phi_I = -36.9^\circ \rightarrow \tilde{I}_1 = 18.1 \angle -36.9^\circ \text{ A}$$

$$\downarrow \Rightarrow \phi_I = -36.9^\circ$$

KVL

$$-V_1 + \tilde{I}_1(1 + j2) + 460 = 0 \Rightarrow V_1 = (18.1 \angle -36.9^\circ)(1 + j2) + 460 = 454.5 \angle 5.03^\circ \text{ V}$$

$\therefore |V_1| = 454.5 \text{ V}$ ← b/c of leading pf, we don't need to drive the XF as hard to see 460V across the primary w/ff.

VOLTAGE REGULATION

$$V.R. = \frac{454.5 - 460}{460} \times 100\% = -1.196\%$$

PROBLEM 6

TWO 250kVA, 230/460V TRANSFORMERS ARE CONNECTED IN AN OPEN DELTA TO SUPPLY A BALANCED 3 ϕ LOAD @ 460V w/ pf = 0.8 lagging.

BY DEF, OPEN Δ CAN ONLY SUPPLY 58% OF WHAT A COMPLETE Δ - Δ CAN.

MAX SECONDARY LINE CURRENT

FOR ONE XF, $S_{rated} = 250 \text{ kVA} + V_{sec} = 460 \text{ V}$.

$$\therefore I_{2,max} = \frac{250 \text{ k}}{460} = 543.5 \text{ A}$$



REAL POWER DELIVERED BY EACH XF

$$P_{ab} = \sqrt{3} V I \cos(30^\circ + \phi) \rightarrow \phi = \cos^{-1}(0.8) = +36.9^\circ$$

$$P_{bc} = \sqrt{3} V I \cos(30^\circ - \phi)$$

$$\rightarrow P_{ab} = (250 \text{ k}) \cos(30^\circ + 36.9^\circ) = 93.1 \text{ kW} = P_{ab}$$

$$\rightarrow P_{bc} = (250 \text{ k}) \cos(30^\circ - 36.9^\circ) = 248.2 \text{ kW} = P_{bc}$$

PRIMARY LINE CURRENTS

CAN FIND I_1 USING TRANS RATIO

$$a = \frac{230}{460} = \frac{1}{2}$$

$$\therefore I_1 = \left(\frac{1}{2}\right) I_2 = 2(543.5)$$

$$\Rightarrow \boxed{I_1 = 1.09 \text{ kA}}$$

% \uparrow OF REAL POWER w/ COMPLETE Δ

$$S_{3\phi} = 3VI = 3S_{1\phi} = 3(250 \text{ k}) = 750 \text{ kVA}$$

$$P = S \cdot \text{pf} \Rightarrow P_{3\phi} = S_{3\phi} \text{pf} = (750 \text{ k})(0.8) = 600 \text{ kW} = P_{3\phi}$$

$$\Delta\% = \frac{P_{new} - P_{old}}{P_{old}} \times 100\% = \frac{600 \text{ kW} - (93.1 \text{ kW} + 248.2 \text{ kW})}{(93.1 \text{ kW} + 248.2 \text{ kW})} \times 100\% = 73.3\% \text{ increase}$$